

Khoa Tran  
EE 371  
April 12, 2021  
Lab 1 Report

## Procedure

### Parking Lot Occupancy Counter

Approaching this problem, I first drew up the block diagram to figure out how to connect each FSM in order to produce the correct output for the number of cars in the parking lot, keeping track of the sensor inputs for either a car is entering or exiting, and connecting the outputs to the inputs of a counter that increments and decrements in order to get an accurate reading of the number of cars in the parking lot. As seen in the block diagram in figure 1, the switches in the GPIO are connected to the inputs of the parking lot finite state machine, and the outputs are the 7 segment HEX board display, and the LEDs of the GPIO.

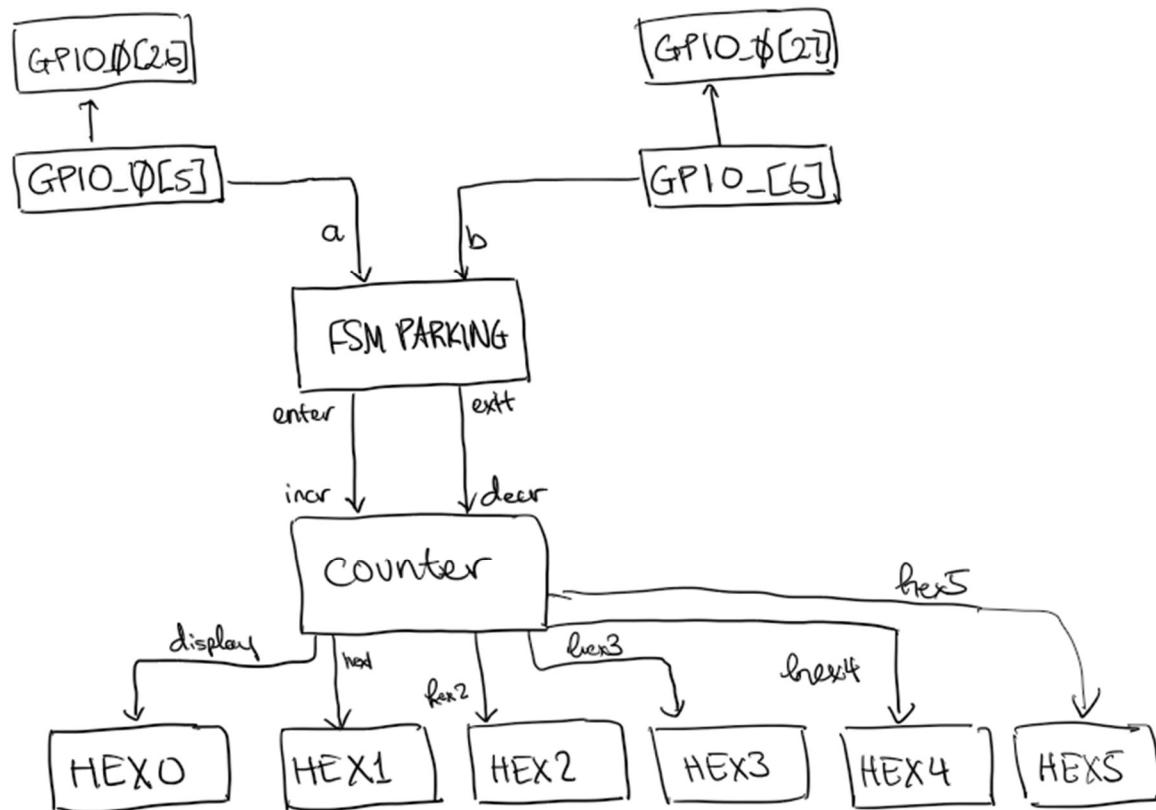


Figure 1: Block diagram for parking lot occupancy counter

### Sensor Input Task

Approaching this problem, I first drew up the state diagram in order to figure out the number of states that I need and when to progress to each state depending on the inputs of `a` and `b` in order to have either `exit` or `enter` be true. As seen in figure 1, when the state diagram goes from `S0` to

S3 and with a 00 input, then the enter output would be 1. Otherwise, if the state diagram goes from S0 to S1 and with the input of 00, the exit output would be 1.

$S_0$  = both sensors unblocked

$S_1$  = a is blocked and b isn't blocked

$S_2$  = both sensors are blocked

$S_3$  = b is blocked and a isn't blocked

 


Figure 2: State diagram for sensor detection of exit and enter

## Counter Task

Approaching this problem, I started by drawing out the state diagram for the counters of 3 bit and 5-bit. Depending on the input of incr and decr, the counter either moves up for incr and down for decr. These values are 1-7 for 3-bit and 31 for 5-bit. However, in this problem, for 3-bit, the maximum capacity of the parking lot is 5 cars, so after 5, the counter will still increment, but the display value will be nothing as it cannot past 5 cars. The same is for 5-bit, as the maximum value is 25, and at that state, the display will be 25, and anything more is nothing. Afterwards, I implemented this design on Verilog with two inputs and six outputs that correspond to the individual 7-segment hex display.

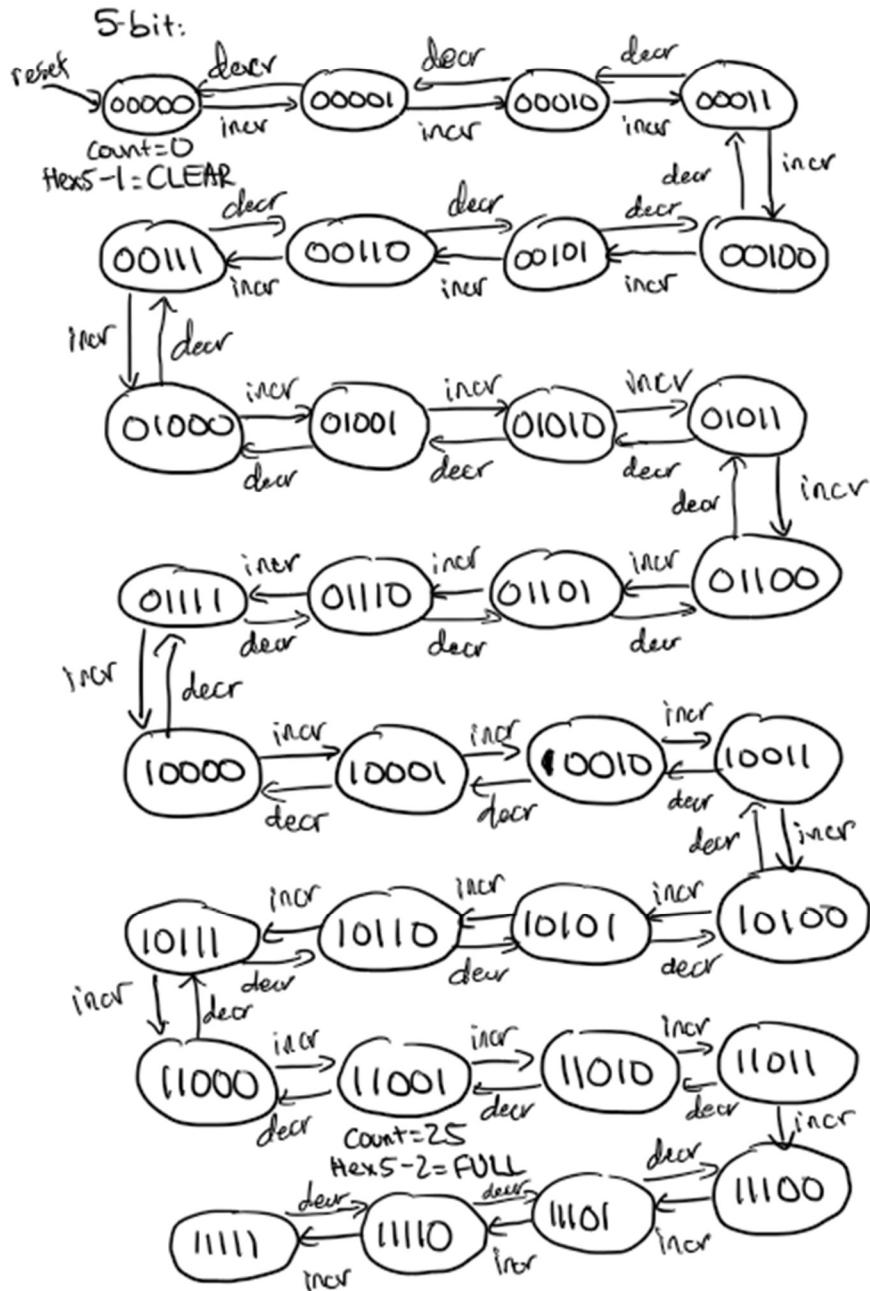
 


Figure 3: State diagram 3- and 5-bit counters

## Results

### Sensor Input Task:

For the first part, I tested if the finite state machine will go through the correct states by checking if enter increments on the input sequence of 10, 11, 01, 00. I also tested for the opposite of enter, the exit output as it should increment on the input sequence of 01, 11, 10, 00. As seen in figure 4, the sequence of inputs produced the correct outputs for both enter and exit. For the simulations, the input and output progresses if the clock is at the positive edge.

 


Figure 4: The waveform generated by the FSM for the Sensor Inputs

### Counter Task:

For this simulation, I tested the inputs of incr and decr in order to check if the values of display, hex1, hex2, hex3, hex4, and hex5 are correct in order to be transferred to the DE1\_SoC module and the 7-segment hex display board. As seen in the waveform generated by the counter module in figure 5, the hex display board starts at “CLEAR0” then progresses to “01” and continues to count when incr is true. It was difficult to fit all the simulations towards the maximum capacity of 25, however, I was able to run the simulation individually, and confirmed the output at the count of 25 to be “FULL25”. As a result, this waveform simulation shows that my counter module works perfectly with the inputs of incr and decr.

 


Figure 5: The waveform generated by the wind module

The size of FSM (fsm parking module) is  $27+7$ , which equals 34. This is the size of the design in terms of FPGA logic and DFF resources with the cost of the clock divider as the cost of the clock divider isn't given.

Analysis & Synthesis Resource Utilization by Entity										
<<Filter>>										
	Compilation Hierarchy Node	Combinational ALUTs	Dedicated Logic Registers	Block Memory Bits	DSP Blocks	Pins	Virtual Pins	Full Hierarchy Name	Entity Name	Library Name
1	DE1_SoC	27 (0)	7 (0)	0	0	87	0	DE1_SoC	DE1_SoC	work
1	[counter:count]	23 (23)	5 (5)	0	0	0	0	DE1_SoC[counter:count]	counter	work
2	[fsm:parking]	4 (4)	2 (2)	0	0	0	0	DE1_SoC[fsm:parking]	fsm	work

Figure 6: Analysis and Synthesis Resource Utilization of the DE1\_SoC

## Final Product

The overarching goal of this project was to design a system that takes in the inputs of two sensors in order to detect the movement of cars going in or out of a parking lot. The goal was also to develop a counter to keep track of the number of cars currently in the parking lot. Overall, this project was designed to fit the goals as it was able to take in the inputs of two switches (sensors) and traverse through the finite state machine in order to determine if a car has entered or exited the parking lot. From then, the counter takes care of the number of cars, incrementing the value when a car enters and decrementing when a car exits. At 25 cars, the hex board displays full and if another car enters then it displays nothing as that is not possible. I was able to develop each part of the design, from the parking lot sensor inputs to the counters, both work in conjunction to develop a parking lot occupancy counter system. The difference on what was asked, and the finished product is minimal as it executed inputs with the correct outputs.

## Appendix: SystemVerilog Code

### 1) fsm.sv

```
1 //Khoa Tran
2 //04/12/2021
3 //CSE 371
4 //Lab 1, Task 1
5 //This module represents the finite state machine for the parking lot as it represents
6 //the input of sensor a and b. As a and b are one-bit inputs, the module goes through
7 //the order of progression of the two inputs in order to determine either an enter or
8 //an exit output value.
9
10 //Implementing the fsm module with the inputs clk, reset, a, and b. The enter and
11 //exit variable outputs are a one-bit value indicating either the parking lot got one
12 //more or less car. This fsm module allows for reset to start the input sequence and
13 //current state over again. Lastly, the module progress to the next input value when clk is
14 //a positive edge.
15 module fsm (clk, reset, a, b, enter, exit);
16     input logic clk, reset; //input for clk, reset
17     input logic a, b; //input for sensor a and b
18     output logic exit; //output for exit
19     output logic enter; //output for enter
20
21     enum {S0, S1, S2, S3} ps, ns; //all five states, present state, next state
22
23     always_comb begin //comb next state logic
24         case (ps)
25             S0: if (a & ~b) ns = S1; //initial state, both sensor is unblocked
26                 else if (~a & b) ns = S3;
27                 else ns = S0;
28             S1: if (a & b) ns = S2; //state of sensor a blocked, and b unblocked
29                 else if (~a & ~b) ns = S0;
30                 else ns = S1;
31             S2: if (a & ~b) ns = S1; //state of both sensors blocked
32                 else if (~a & b) ns = S3;
33                 else ns = S2;
34             S3: if (a & b) ns = S2; //state of sensor b blocked, and a unblocked
35                 else if (~a & ~b) ns = S0;
36                 else ns = S3;
37         endcase
38     end
39
40     // equation for output of enter and exit as it depends on present state and input, a and
41     // b.
42     assign enter = ((ps == S3) & ~a & ~b);
43     assign exit = ((ps == S1) & ~a & ~b);
44
45     //sequential logic (DFFs)
46     always_ff @(posedge clk) begin
47         if (reset)
48             ps <= S0;
49         else
50             ps <= ns;
51     end
52 endmodule
53
54 //Module test the output of the fsm module by running a sequence of inputs
55 //on a and b and testing if the output, enter and exit, is correct.
56 module fsm_testbench();
57     logic clk, reset, a, b, enter, exit;
58
59     //devices under test
60     fsm dut (.clk, .reset, .a, .b, .enter, .exit);
61
62     //clock setup
63     parameter clock_period = 100;
64
65     initial begin
66         clk <= 0;
67         forever #(clock_period /2) clk <= ~clk;
68     end
69
70     //initial simulation
71     initial begin
72         reset <= 1;
73         reset <= 0; a<=0; b<=0; @ (posedge clk);
74         reset <= 0; a<=1; b<=0; @ (posedge clk);
75         reset <= 0; a<=1; b<=1; @ (posedge clk);
76         reset <= 0; a<=0; b<=1; @ (posedge clk);
77         reset <= 0; a<=0; b<=0; @ (posedge clk);
78         reset <= 0; a<=0; b<=1; @ (posedge clk);
79         reset <= 0; a<=1; b<=1; @ (posedge clk);
80         reset <= 0; a<=1; b<=0; @ (posedge clk);
81         reset <= 0; a<=0; b<=0; @ (posedge clk);
82         reset <= 0; a<=0; b<=1; @ (posedge clk);
83     end
84
85     $stop; //end simulation
86 end
87 endmodule
88
89
```

```
75     reset <= 0; a<=0; b<=0; @ (posedge clk);
76     reset <= 0; a<=1; b<=0; @ (posedge clk);
77     reset <= 0; a<=1; b<=1; @ (posedge clk);
78     reset <= 0; a<=0; b<=1; @ (posedge clk);
79     reset <= 0; a<=0; b<=0; @ (posedge clk);
80     reset <= 0; a<=0; b<=1; @ (posedge clk);
81     reset <= 0; a<=1; b<=1; @ (posedge clk);
82     reset <= 0; a<=1; b<=0; @ (posedge clk);
83     reset <= 0; a<=0; b<=0; @ (posedge clk);
84     reset <= 0; a<=0; b<=1; @ (posedge clk);
85
86     $stop; //end simulation
87 end
88 endmodule
89
```

## 2) counter.sv

```
1 //khoa Tran
2 //04/12/2021
3 //CSE 371
4 //Lab 1: Counter Task 2
5 //This module implements a sequential circuit that acts as a register
6 //that goes through a specific state sequence. In this module, it is a
7 //counter that has a specific n-bit size, and counts from 0 to 2^n-1
8 //in binary. This module counts upwards at positive clock edge. This
9 //module allows reset to make the output go back to 0 when reset is called.
10 //As the counter increases or decreases, the 7-bit values for the display of hex0
11 //to hex5 is given in a combinational circuit in order to display the current
12 //number of cars in the parking lot. At 0 cars, the display is "CLEAR0" and at 25
13 //cars, it displays "FULL25". For all other values, it will just display the value.
14
15 //Implements counter module with input incr, decr, reset, clk, display, hex1, hex2,
16 //hex3, hex4, and hex5, along with a parameter to initialize the n-bit size desired.
17 //The output variable is display and hex1 through hex5, which are the outputs
18 //to the display on the 7-segment HEX board as it shows the current count of cars
19 //incrementing when incr is 1 and decrementing when decr is 1. This module counts from 0 to
20 2^n-1
21 //in binary and counts upwards at positive clock edge. This
22 //module allows reset to make the output go back to 0 when reset is called. As the
23 //counter's count
24 //increase or decrease, the display outputs the 7-bit binary output for the HEX board
25 //displaying the current digital value, when the binary value equals 25.
26 //the parking lot is full and shows a message displaying that.
27 module counter #(parameter width = 5) (incr, decr, reset, clk, display, hex1, hex2, hex3,
28 hex4, hex5);
29 logic [width-1:0] out; //current value
30 input logic incr, decr, reset, clk; //input incr, decr, reset, and clk
31 output logic [6:0] display; //outputs for HEX0-5
32 output logic [6:0] hex1;
33 output logic [6:0] hex2;
34 output logic [6:0] hex3;
35 output logic [6:0] hex4;
36 output logic [6:0] hex5;
37
38 //7-seg hex display for values zero through nine
39 logic [6:0] zero, one, two, three, four, five, six, seven, eight, nine;
40 assign zero = 7'b1000000;
41 assign one = 7'b1111111;
42 assign two = 7'b0100100;
43 assign three = 7'b0110000;
44 assign four = 7'b0011001;
45 assign five = 7'b0010010;
46 assign six = 7'b0000010;
47 assign seven = 7'b1111000;
48 assign eight = 7'b0000000;
49 assign nine = 7'b0100000;
50
51 //sequential (DFFs) incr and decr out
52 always_ff @(posedge clk)
53 begin
54 if (reset)
55 out <= 0;
56 else if (incr)
57 out <= out + 1;
58 else if (decr)
59 out <= out - 1;
60 end
61
62 //combinational for cases of out values 1-25
63 always_comb begin
64 case (out)
65 5'b00000: begin //0 (CLEAR0)
66 hex5 = 7'b1000110;
67 hex4 = 7'b1000110;
68 hex3 = 7'b0000010;
69 hex2 = 7'b0001000;
70 hex1 = 7'b0101111;
71 display = zero;
72 end
73 5'b00001: begin
74 hex5 = 7'b1111111;
75 hex4 = 7'b1111111;
76 hex3 = 7'b1111111;
77 hex2 = 7'b1111111;
78 hex1 = 7'b1111111;
79 display = one;
80 end
81 5'b00010: begin
82 hex5 = 7'b1111111;
83 hex4 = 7'b1111111;
84 hex3 = 7'b1111111;
85 hex2 = 7'b1111111;
86 hex1 = 7'b1111111;
87 display = two;
88 end
89 5'b00011: begin
90 hex5 = 7'b1111111;
91 hex4 = 7'b1111111;
92 hex3 = 7'b1111111;
93 hex2 = 7'b1111111;
94 hex1 = 7'b1111111;
95 display = three;
96 end
97 5'b00100: begin
98 hex5 = 7'b1111111;
99 hex4 = 7'b1111111;
100 hex3 = 7'b1111111;
101 hex2 = 7'b1111111;
102 hex1 = 7'b1111111;
103 display = four;
104 end
105 5'b00101: begin
106 hex5 = 7'b1111111;
107 hex4 = 7'b1111111;
108 hex3 = 7'b1111111;
109 hex2 = 7'b1111111;
110 hex1 = 7'b1111111;
111 display = five;
112 end
113 5'b00110: begin
114 hex5 = 7'b1111111;
115 hex4 = 7'b1111111;
116 hex3 = 7'b1111111;
117 hex2 = 7'b1111111;
118 hex1 = 7'b1111111;
119 display = six;
120 end
121 5'b00111: begin
122 hex5 = 7'b1111111;
123 hex4 = 7'b1111111;
124 hex3 = 7'b1111111;
125 hex2 = 7'b1111111;
126 hex1 = 7'b1111111;
127 display = seven;
128 end
129 5'b01000: begin
130 hex5 = 7'b1111111;
131 hex4 = 7'b1111111;
132 hex3 = 7'b1111111;
133 hex2 = 7'b1111111;
134 hex1 = 7'b1111111;
135 display = eight;
136 end
137 5'b01001: begin
138 hex5 = 7'b1111111;
139 hex4 = 7'b1111111;
140 hex3 = 7'b1111111;
141 hex2 = 7'b1111111;
142 hex1 = 7'b1111111;
143 display = nine;
144 end
145 5'b01010: begin
146 hex5 = 7'b1111111;
147 hex4 = 7'b1111111;
148 hex3 = 7'b1111111;
149 hex2 = 7'b1111111;
150 hex1 = 7'b1111111;
151 display = zero;
152 end
153 end
```



```

150      S'b01011: begin
151          hex5 = 7'b1111111;
152          hex4 = 7'b1111111;
153          hex3 = 7'b1111111;
154          hex2 = 7'b1111111;
155          hex1 = one;
156          display = one;
157      end
158      S'b01100: begin
159          hex5 = 7'b1111111;
160          hex4 = 7'b1111111;
161          hex3 = 7'b1111111;
162          hex2 = 7'b1111111;
163          hex1 = one;
164          display = two;
165      end
166      S'b01101: begin
167          hex5 = 7'b1111111;
168          hex4 = 7'b1111111;
169          hex3 = 7'b1111111;
170          hex2 = 7'b1111111;
171          hex1 = one;
172          display = three;
173      end
174      S'b01110: begin
175          hex5 = 7'b1111111;
176          hex4 = 7'b1111111;
177          hex3 = 7'b1111111;
178          hex2 = 7'b1111111;
179          hex1 = one;
180          display = four;
181      end
182      S'b01111: begin
183          hex5 = 7'b1111111;
184          hex4 = 7'b1111111;
185          hex3 = 7'b1111111;
186          hex2 = 7'b1111111;
187          hex1 = one;
188          display = five;
189      end
190      S'b10000: begin
191          hex5 = 7'b1111111;
192          hex4 = 7'b1111111;
193          hex3 = 7'b1111111;
194          hex2 = 7'b1111111;
195          hex1 = one;
196          display = six;
197      end
198      S'b10001: begin
199          hex5 = 7'b1111111;
200          hex4 = 7'b1111111;
201          hex3 = 7'b1111111;
202          hex2 = 7'b1111111;
203          hex1 = one;
204          display = seven;
205      end
206      S'b10010: begin
207          hex5 = 7'b1111111;
208          hex4 = 7'b1111111;
209          hex3 = 7'b1111111;
210          hex2 = 7'b1111111;
211          hex1 = one;
212          display = eight;
213      end
214      S'b10011: begin
215          hex5 = 7'b1111111;
216          hex4 = 7'b1111111;
217          hex3 = 7'b1111111;
218          hex2 = 7'b1111111;
219          hex1 = one;
220          display = nine;
221      end
222      S'b10100: begin
223          hex5 = 7'b1111111;
224          hex4 = 7'b1111111;
225          hex3 = 7'b1111111;

```

Page 3 of 5

Revision: DE1\_SoC

Date: April 12, 2021

counter.v

Project: DE1\_SoC

```

226          hex2 = 7'b1111111;
227          hex1 = two;
228          display = zero;
229      end
230      S'b10101: begin
231          hex5 = 7'b1111111;
232          hex4 = 7'b1111111;
233          hex3 = 7'b1111111;
234          hex2 = 7'b1111111;
235          hex1 = two;
236          display = one;
237      end
238      S'b10110: begin
239          hex5 = 7'b1111111;
240          hex4 = 7'b1111111;
241          hex3 = 7'b1111111;
242          hex2 = 7'b1111111;
243          hex1 = two;
244          display = two;
245      end
246      S'b10111: begin
247          hex5 = 7'b1111111;
248          hex4 = 7'b1111111;
249          hex3 = 7'b1111111;
250          hex2 = 7'b1111111;
251          hex1 = two;
252          display = three;
253      end
254      S'b11000: begin
255          hex5 = 7'b1111111;
256          hex4 = 7'b1111111;
257          hex3 = 7'b1111111;
258          hex2 = 7'b1111111;
259          hex1 = two;
260          display = four;
261      end
262      S'b11001: begin //25 (FULL25)
263          hex5 = 7'b0001110;
264          hex4 = 7'b1000001;
265          hex3 = 7'b1000111;
266          hex2 = 7'b1000111;
267          hex1 = two;
268          display = five;
269      end
270      default: begin
271          hex5 = 7'b1111111;
272          hex4 = 7'b1111111;
273          hex3 = 7'b1111111;
274          hex2 = 7'b1111111;
275          hex1 = 7'b1111111;
276          display = 7'b1111111;
277      end
278  endcase
279  end
280 endmodule

```



```

281
282 //Module test the output of the counter module by running a sequence of inputs
283 //on reset, incr and decr to test if the output of display, hex1, hex2, hex3, hex4, and hex5.
284 //is correct along the positive edges, by making sure out counts up by 1 when incr is 1 and
285 //decrements when decr is 1.
286 module counter_testbench#(parameter width = 5)();
287
288     logic incr, decr, reset, clk;
289     logic [6:0] display;
290     logic [6:0] hex1;
291     logic [6:0] hex2;
292     logic [6:0] hex3;
293     logic [6:0] hex4;
294     logic [6:0] hex5;
295     logic [width - 1:0] out;
296
297     //devices under test
298     counter dut (.incr, .decr, .reset, .clk, .display, .hex1, .hex2, .hex3, .hex4, .hex5);
299
300     //clock setup
301     parameter clock_period = 100;

```

```

302
303     initial begin
304         clk <= 0;
305         forever #(clock_period / 2) clk <= ~clk;
306     end
307     //initial simulation
308     initial begin
309         reset <= 1;
310         reset <= 0; incr<=0; decr<=0; @ (posedge clk);
311         reset <= 0; incr<=1; decr<=0; @ (posedge clk);
312         reset <= 0; incr<=1; decr<=0; @ (posedge clk);
313         reset <= 0; incr<=1; decr<=0; @ (posedge clk);
314         reset <= 0; incr<=1; decr<=0; @ (posedge clk);
315         reset <= 0; incr<=1; decr<=0; @ (posedge clk);
316         reset <= 0; incr<=0; decr<=1; @ (posedge clk);
317         reset <= 0; incr<=0; decr<=1; @ (posedge clk);
318         reset <= 0; incr<=0; decr<=1; @ (posedge clk);
319         reset <= 0; incr<=0; decr<=1; @ (posedge clk);
320         reset <= 0; incr<=0; decr<=1; @ (posedge clk);
321         reset <= 0; incr<=0; decr<=1; @ (posedge clk);
322
323         $stop; //end simulation
324     end
325 endmodule
326

```

### 3) DE1\_SoC.sv

```

1 //Khoa Tran
2 //04/12/2021
3 //CSE 371
4 //Lab 1, DE1_SoC Task3
5 //This module, DE1_SoC takes the inout switches of the GPIO_0, Clock_50 input,
6 //in order to have the switches be connected to the LED on the breadboard. These
7 //switches are connected to the fsm of the parking lot problem, as the first GPIO
8 //switch is connected to input a, and the other switch connected to input b.
9 //From these inputs, the fsm will output a value for the counter to either increment
10 //or decrement. Afterwards, the output of the counter indicates the amount of cars in the
11 //lot, displaying the values on the hex 7-segment display. The reset is connected to
12 //the third switch on the breadboard, allowing the state of the parking lot to go back
13 //to zero cars. Additionally, implements a clock that is connected to LEDR[5] and will
14 //express the input whenever the clock, and led is on with the positive edge.
15 module DE1_SoC (CLOCK_50, HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, LEDR, GPIO_0);
16     input logic CLOCK_50; // 50MHz clock
17     output logic [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
18     output logic [9:0] LEDR;
19
20     inout logic [33:0] GPIO_0;
21
22
23     logic reset;
24     logic [31:0] div_clk;
25
26     assign reset = GPIO_0[7]; //third switch connected to reset
27     parameter whichClock = 22; // 0.75 Hz clock
28
29     assign GPIO_0[26] = GPIO_0[5]; //connecting switches to leds
30     assign GPIO_0[27] = GPIO_0[6];
31
32     clock_divider cdv (.clock(CLOCK_50), .reset(reset), .divided_clocks(div_clk));
33
34     logic clkSelect;
35
36     assign clkSelect = CLOCK_50; // for simulation
37
38     //assign clkSelect = div_clk[whichClock]; // for board
39
40     //LEDR[0] connected to clk
41     assign LEDR[0] = clkSelect;
42
43     // logic variables for output of fsm
44     logic enterOut;
45     logic exitOut;
46
47     fsm parking(.clk(clkSelect), .reset(reset), .a(GPIO_0[5]), .b(GPIO_0[6]), .enter(enterOut
48 ), .exit(exitOut));
49     //output of fsm goes into counter for count and display of values
50     counter count(.incr(enterOut), .decr(exitOut), .reset(reset), .clk(clkSelect), .display(
51 HEX0), .hex1(HEX1), .hex2(HEX2), .hex3(HEX3), .hex4(HEX4), .hex5(HEX5));
52
53 endmodule
54
55 //Module test the output of the DE1_SoC module by running a sequence of inputs
56 //on the switches on the GPIO[5] and GPIO[6] and GPIO[7] as the reset
57 //in order to test if the output on the HEX0, HEX1, HEX2, HEX3, HEX4, and HEX5
58 //is correct along the positive edges.
59 module DE1_SoC_testbench();
60     logic CLOCK_50;
61     logic [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
62     logic [9:0] LEDR;
63     wire [33:0] GPIO_0;
64     logic Sw0, Sw1, reset;
65
66     DE1_SoC dut (.CLOCK_50, .HEX0, .HEX1, .HEX2, .HEX3, .HEX4, .HEX5, .LEDR, .GPIO_0);
67
68     assign GPIO_0[5] = Sw0;
69     assign GPIO_0[6] = Sw1;
70     assign GPIO_0[7] = reset;
71
72     parameter clock_period = 100;
73
74     initial begin
75         CLOCK_50 <= 0;
76         forever #(clock_period / 2) CLOCK_50 <= ~CLOCK_50;
77     end //initial
78
79     initial begin
80         reset <= 1; @(posedge CLOCK_50);
81         reset <= 0; @(posedge CLOCK_50);
82
83         Sw0 <= 0; Sw1 <= 0; @(posedge CLOCK_50);
84         Sw0 <= 1; Sw1 <= 0; @(posedge CLOCK_50);
85         Sw0 <= 1; Sw1 <= 1; @(posedge CLOCK_50);
86         Sw0 <= 0; Sw1 <= 1; @(posedge CLOCK_50);
87         Sw0 <= 0; Sw1 <= 0; @(posedge CLOCK_50);
88         Sw0 <= 1; Sw1 <= 0; @(posedge CLOCK_50);
89         Sw0 <= 1; Sw1 <= 1; @(posedge CLOCK_50);
90         Sw0 <= 0; Sw1 <= 1; @(posedge CLOCK_50);
91         Sw0 <= 0; Sw1 <= 0; @(posedge CLOCK_50);
92         Sw0 <= 0; Sw1 <= 1; @(posedge CLOCK_50);
93         Sw0 <= 1; Sw1 <= 1; @(posedge CLOCK_50);
94         Sw0 <= 1; Sw1 <= 0; @(posedge CLOCK_50);
95         Sw0 <= 0; Sw1 <= 0; @(posedge CLOCK_50);
96         Sw0 <= 0; Sw1 <= 1; @(posedge CLOCK_50);
97         Sw0 <= 0; Sw1 <= 0; @(posedge CLOCK_50);
98
99     $stop;
100 end
101
102 endmodule
103
104 //clock_divider module has inputs of the clock, reset, and the
105 //32 bit divided_clock which allows to sequence through and
106 //output whenever the positive edge has been reached on the clock
107 //divided_clocks[0] = 25MHz, [1] = 12.5MHz, [23] = 3Hz, [24] = 1.5Hz, [25] = 0.75Hz, ...
108 module clock_divider (clock, reset, divided_clocks);
109     input logic reset, clock;
110     output logic [31:0] divided_clocks = 0;
111
112     always_ff @(posedge clock) begin
113         divided_clocks <= divided_clocks + 1;
114     end
115
116 endmodule

```